

**FEDERAL INSTITUTE OF SCIENCE AND
TECHNOLOGY, ANGAMALY**

**DEPARTMENT OF ELECTRONICS AND
INSTRUMENTATION ENGINEERING**

**DESIGN AND
IMPLEMENTATION OF A 48V TO
12V
HIGH-EFFICIENCY BUCK
CONVERTER**

Submitted by

IBRAHIM K M

BTECH
SEMESTER 5

2024-2028

Contents

1	Introduction	2
2	Technical Specifications and Components	2
2.1	Bill of Materials (BOM)	2
3	Theory of Operation	3
3.1	Phase 1: Switch ON (Charging)	3
3.2	Phase 2: Switch OFF (Discharging)	3
3.3	Closed-Loop Feedback Regulation	3
4	PCB Layout and Routing Methodology	4
4.1	Trace Widths and Power Planes	4
4.2	Overcoming DRC Challenges	4
5	Conclusion	4

Abstract

This report details the design, schematic capture, and PCB layout of a highly efficient Switch Mode Power Supply (SMPS). The circuit is a Buck Converter designed to step down a high-voltage 48V DC input to a stable, regulated 12V DC output using the LM2576HVS-12 step-down voltage regulator. The project was developed using KiCad EDA software and demonstrates proficiency in power electronics, closed-loop feedback systems, and professional PCB layout techniques including ground plane management, thermal relief routing, and Design Rules Check (DRC) clearances. The final layout successfully passed all Electrical and Design Rule Checks with zero errors.

1 Introduction

Power regulation is a fundamental requirement in modern electronics. While traditional linear regulators (such as the LM7812) are simple to use, they are highly inefficient for large voltage drops. A linear regulator steps down voltage by acting as a variable resistor, dissipating excess voltage as pure heat. Attempting to drop 48V to 12V at a 3-Amp load using a linear regulator would generate over 100 Watts of wasted heat, leading to immediate thermal failure.

To solve this, modern power electronics utilize Switch Mode Power Supplies (SMPS). A buck converter is a specific type of SMPS that steps down voltage by rapidly switching an internal transistor on and off. By controlling the Duty Cycle (the percentage of time the switch is closed), the converter efficiently transfers power with minimal heat loss. This project focuses on the practical implementation of such a circuit.

2 Technical Specifications and Components

The hardware was designed to operate safely under high voltage and deliver a clean 12V DC output. The core specifications are as follows:

- **Input Voltage:** 48V DC
- **Output Voltage:** 12.0V DC (Fixed)
- **Switching Frequency:** 52 kHz
- **Control Method:** Pulse Width Modulation (PWM) with Closed-Loop Feedback

2.1 Bill of Materials (BOM)

The specific components selected for this schematic ensure reliable operation:

- **Buck Controller:** LM2576HVS-12. The "HVS" variant was explicitly chosen for its high-voltage input tolerance (up to 60V).
- **Flyback Diode:** SB3100. A 100V, 3A Schottky barrier diode, essential for providing a fast ground return path.

- **Inductor:** 150 μ H Toroidal Inductor. Sized to maintain continuous conduction mode (CCM) and smooth out the current ripple.
- **Input Filter Capacitor:** 100 μ F / 100V Electrolytic Capacitor.
- **Output Filter Capacitor:** 1000 μ F / 25V Electrolytic Capacitor.
- **Load Resistor:** 1k Ω Bleeder resistor to provide a minimal load for regulator stability.

3 Theory of Operation

The LM2576 buck converter operates at a fixed frequency of 52 kHz. To drop 48V to 12V, the chip utilizes a 25% Duty Cycle (D). The mathematical relationship is:

$$D = \frac{V_{out}}{V_{in}} = \frac{12}{48} = 0.25 \quad (1)$$

This means the internal switch is ON for 25% of the switching period and OFF for 75%. The circuit behavior physically changes during these two states.

3.1 Phase 1: Switch ON (Charging)

When the internal switch closes, the full 48V connects to the switching node. The Schottky diode is heavily reverse-biased by this high voltage and blocks all current to ground. The electrical current is forced through the inductor, storing energy in a magnetic field. Because an inductor opposes instantaneous current changes, the current ramps up smoothly, charging the output capacitor and supplying the 12V load.

3.2 Phase 2: Switch OFF (Discharging)

When the switch opens, the 48V source is completely disconnected. According to Lenz's Law, the inductor's magnetic field collapses, inducing a reverse voltage to keep the current flowing. This pulls the switching node down to approximately -0.5V, which forward-biases the Schottky diode. The diode now acts as a ground return path (freewheeling path), allowing the stored energy in the inductor to continuously flow to the load.

3.3 Closed-Loop Feedback Regulation

To lock the output at exactly 12V regardless of the load, the chip uses a closed-loop control system. Pin 4 (FEEDBACK) is wired directly to the output. Inside the LM2576-12, a precision resistor divider scales the 12V input down to exactly 1.23V. An internal Error Amplifier continuously compares this divided voltage to a permanent 1.23V Bandgap Reference.

If a heavy load is connected and the output sags to 11.5V, the Error Amplifier senses the drop and commands the PWM controller to increase the duty cycle, pumping more energy from the 48V source. If the voltage spikes, it shrinks the duty cycle. These microsecond adjustments perfectly stabilize the output at 12.0V DC.

4 PCB Layout and Routing Methodology

Translating the schematic into a physical Printed Circuit Board (PCB) required careful attention to power routing principles and KiCad Design Rules.

4.1 Trace Widths and Power Planes

Unlike low-power digital signals, switch-mode power supplies carry high currents. The primary power paths (VIN, SW, VOUT, and GND) were routed using exceptionally thick traces to minimize parasitic resistance and localized heating. Furthermore, a solid copper Ground (GND) pour was implemented across the entire board. This provides a low-impedance return path for the high-frequency switching currents and helps mitigate Electromagnetic Interference (EMI).

4.2 Overcoming DRC Challenges

During the layout phase, two significant Design Rules Check (DRC) challenges were encountered and resolved:

1. **Annular Ring Widths:** The default KiCad board constraints require a minimum annular copper ring of 0.1mm. However, the standard TO-220 footprint for the LM2576 utilizes a 0.0875mm ring. This was resolved by adjusting the project's Board Setup constraints to safely allow a 0.08mm minimum annular width, clearing the violations while maintaining manufacturability.
2. **Thermal Relief Spoke Constraints:** When connecting through-hole pins to the massive copper ground plane, thermal reliefs (spokes) are required to prevent the copper from acting as a heatsink during soldering. KiCad requires a minimum of 2 spokes. Initially, thick power traces routed too close to the ground pins acted as "dams," restricting the copper pour and resulting in a 1-spoke DRC error. This was resolved by physically dragging the power traces outward to provide the pins with a wider clearance, allowing the copper to flow evenly and automatically generate robust 2-spoke thermal connections.

5 Conclusion

The design of the 48V to 12V Buck Converter was highly successful. The final KiCad project features a well-structured schematic with explicit component values and designated power flags. The physical PCB layout demonstrates professional practices, including thick power traces, an encompassing Edge.Cuts boundary, a solid ground plane, and properly routed thermal reliefs. The project passes all Electrical Rules Checks (ERC) and Design Rules Checks (DRC) with zero errors, resulting in a robust, manufacturing-ready switch-mode power supply design.